



Miller Experiment 6

1. Table 6-1 Addition Results

SUM	Carry Out
111	0
1	1
1010	0
1110	1
1000	0

1. L(1), L(5)
2. 11111

Table 6-2 Subtraction Results

DIFFERENCE	BORROW
1001	0
111	1
0	1
1100	1
1100	0
111	1
111	0

3. L(6)

4. High Sub

5. Difference of A \rightarrow B = 9

6. Xors produce 1's complement of each bit and is then added to corresponding input.